

## PROBLEM SET 9

Due: 24 November 2016, 2 p.m.

**Problem 1.** In a *perfect conductor*, the conductivity is infinite, so  $\mathbf{E} = 0$ , and any net charge resides on the surface (just as it does for an imperfect conductor in *electrostatics*). (a) Show that the magnetic field is constant, *i.e.*  $\frac{\partial \mathbf{B}}{\partial t} = 0$ , inside a perfect conductor. (b) Show that the magnetic flux through a perfectly conducting loop is constant.

(2 + 2 marks)

**Problem 2.** A *superconductor* is a perfect conductor with the additional property that the (constant) magnetic field  $\mathbf{B}$  inside is in fact zero. (This "flux exclusion", known as the Meissner effect, was shown in one of the videos we watched in class.)


Show that the electric current in a superconductor is confined to the surface.

(2 marks)

**Problem 3.** Consider two light bulbs connected in series around a solenoid (see figure (A)) producing a sinusoidally varying magnetic field. If we alter the circuit by connecting a thick copper wire across the circuit (see figure (B)), we find that the top bulb gets much brighter and the bottom one no longer glows.

Why does this happen?

(2 marks)

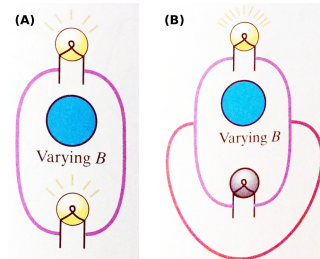


**Problem 4.** Consider a circuit shown in the figure below. The current in a long solenoid piercing the plane of the circuit is increasing linearly with time, so that the magnetic flux through the cross-section of the solenoid  $\Phi_B = \alpha t$ . Two voltmeters are connected to diametrically opposite points  $A$  and  $B$ , together with resistors  $R_1$  and  $R_2$ .

Show that the readings on voltmeters are  $V_1 = \frac{\alpha R_1}{R_1 + R_2}$  and  $V_2 = -\frac{\alpha R_2}{R_1 + R_2}$ , respectively, *i.e.*  $V_1 \neq V_2$ , even though they are connected to the same points.

Assume that these are ideal voltmeters that draw negligible current (*i.e.* have huge resistance), and that a voltmeter registers  $\int_a^b \mathbf{E} \cdot d\mathbf{l}$  between the terminals and through the meter.


(3 marks)

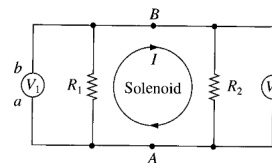

**Problem 5.** Two coils are wrapped around a cylindrical form in such a way that the same flux passes through every turn of both coils. (In practice this is achieved by inserting an iron core through the cylinder; this has the effect of concentrating the flux.) The "primary" coil has  $N_1$  turns and the "secondary" has  $N_2$ . If the current  $I$  in the primary is changing, show that the emf in the secondary is given by  $\mathcal{E}_2/\mathcal{E}_1 = N_2/N_1$ , where  $\mathcal{E}_1$  is the (back emf) of the primary.


This is a primitive transformer — a device for raising or lowering the emf of an alternating current source. By choosing the appropriate number of turns, any desired secondary emf can be achieved.

(2 marks)

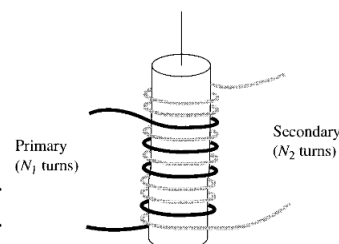

**Problem 6.** Two coils are wrapped around each other as shown in the figure below. The current travels in the same sense around each coil. One coil has self-inductance  $L_1$ , and the other coil has self-inductance  $L_2$ . The mutual inductance of the two coils is  $M$ . Show that if the two coils are connected in parallel, the equivalent inductance of the combination is  $L = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$ .

(3 marks)

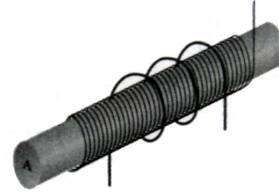

**Problem 7.** A transformer takes an input AC voltage of amplitude  $V_1$ , and delivers an output voltage of amplitude  $V_2$ , which is determined by the turns ratio,  $V_2/V_1 = N_2/N_1$ . If  $N_2 > N_1$  the output voltage is greater than the input voltage. Why doesn't this violate conservation of energy? *Answer:* Power is the product of voltage and current; evidently if the voltage goes up, the current must come down.

The purpose of this problem is to see exactly how this works out, in a simplified model.

(a) In an ideal transformer the same flux passes through all turns of the primary and of the secondary. Show that in this case  $M^2 = L_1 L_2$ , where  $M$  is the mutual inductance of the coils and  $L_1, L_2$  are their individual self-inductances.

(b) Suppose the primary is driven with AC voltage  $V_{\text{in}} = V_1 \cos \omega t$ , and the secondary connected to a resistor with resistance  $R$ . Show that the two currents satisfy the relations

$$L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} = V_1 \cos \omega t, \quad L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = -I_2 R.$$

(c) Using the result in (a) solve the equations for  $I_1$  and  $I_2$ . (Assume that  $I_1$  has no DC component.)

(d) Show that the output voltage  $V_{\text{out}} = I_2 R$  divided by the input voltage  $V_{\text{in}}$  is equal to the turns ratio, *i.e.*  $V_{\text{out}}/V_{\text{in}} = N_2/N_1$ .

(e) Calculate the input power  $P_{\text{in}} = V_{\text{in}} I_1$  and the output power  $P_{\text{out}} = V_{\text{out}} I_2$ , and show that their averages over a full cycle are equal.

(3/2 + 1 + 2 + 1 + 3/2 marks)

**Problem 8.** In the circuit shown in the figure below, switch  $S$  is closed at time  $t = 0$  with no charge initially on the capacitor.

(a) Find the reading of each ammeter and each voltmeter just after  $S$  is closed.

(b) Find the reading of each meter after a long time has elapsed.

(c) Find the maximum charge on the capacitor.

(d) Sketch a qualitative graph of the reading of voltmeter  $V_2$  as a function of time.

(4 × 1 marks)

