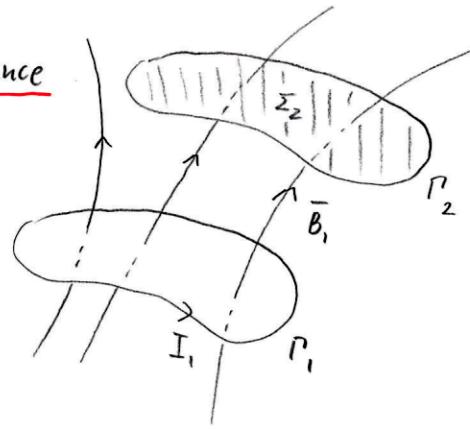


INDUCTANCE

Mutual Inductance



I_1 in $P_1 \Rightarrow \bar{B}_1 \Rightarrow \Phi_{B,2}$ flux through
 Σ_2 bounded by P_2

final $\Phi_{B,2}$



Biot and Savart

$$\bar{B}_1 = \frac{\mu_0}{4\pi} \oint_{P_1} I_1 \frac{d\bar{l}_1 \times (\bar{r} - \bar{r}')}{|\bar{r} - \bar{r}'|^3} \propto I_1$$

$$\Phi_{B,2} = \int_{\Sigma_2} \bar{B}_1 \cdot d\bar{s} \propto I_1$$

\hookrightarrow element of surface

Hence

$$\Phi_{B,2} = (M_{21}) I_1$$

\hookrightarrow mutual inductance

Note. $\Phi_{B,2} = \int_{\Sigma_2} \bar{B}_1 \cdot d\bar{s} = \int_{\Sigma_2} (\nabla \times \bar{A}_1) \cdot d\bar{s} \stackrel{\text{Stokes}}{=} \oint_{P_2} \bar{A}_1 \cdot d\bar{l}_2$

\hookrightarrow vector potential

But (see problem set 8; recall $dI = \bar{J} \cdot d\bar{s}$)

$$\bar{A}_1 = \frac{\mu_0 I_1}{4\pi} \oint_{P_1} \frac{d\bar{l}_1}{|\bar{r} - \bar{r}'|}$$

Hence

$$\Phi_{B,2} = \frac{\mu_0 I_1}{4\pi} \oint_{P_2} \left(\oint_{P_1} \frac{d\bar{l}_1}{|\bar{r} - \bar{r}'|} \right) d\bar{l}_2 = \underbrace{\frac{\mu_0}{4\pi} \oint_{P_2} \left(\oint_{P_1} \frac{d\bar{l}_1}{|\bar{r} - \bar{r}'|} \right) d\bar{l}_2}_{M_{21}} I_1$$

$$M_{21} = \frac{\mu_0}{4\pi} \oint_{P_2} \oint_{P_1} \frac{d\bar{l}_1}{|\bar{r} - \bar{r}'|} d\bar{l}_2$$

Neumann's formula

(units of M_{21} : henry (H))

$$H = \frac{Wb}{A} = \frac{V \cdot s}{A} = \frac{2}{A^2}$$


Comments

- (1) Not very useful for practical calculations
- (2) M_{21} depends only on geometry of the system (sizes/shapes) relative positions of the loops)
- (3) $M_{21} = M_{12}$ (see Neumann's formula). Hence $M_{21} = M_{12} = M$

$$\Phi_{B,2} = M_{21} I_1 = M_{12} I_1 = \Phi_{B,1} \quad \begin{matrix} \hookrightarrow \\ \text{mutual inductance} \end{matrix}$$

(same current)

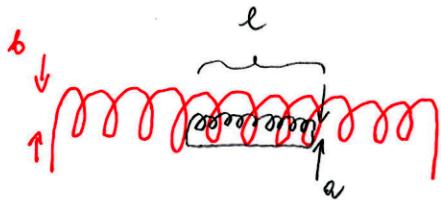Example short solenoid (length l ; radius a ; n_1 turns per unit length) inside a long solenoid (radius b ; n_2 turns per unit length)
 Current I flows through the short solenoid. Find the flux through the long one.



Problem: magnetic field due to the short solenoid - complicated.

Ideas:

$$\Phi_{B, \text{long}} = M_{\text{long, short}} I = \mu_{\text{short, long}} I = \Phi_{B, \text{short}} = B \cdot \pi a^2 \cdot n_1 l$$

↓
 through the
 short one ↓
 through the
 long one ↓
 due
 to the long one

Magnetic field inside the long solenoid

$$B = \mu_0 I n_2$$

Hence

$$\Phi_{B, \text{long}} = \mu_0 I n_2 \pi a^2 n_1 l = \underbrace{\mu_0 \pi a^2 n_1 n_2 l}_M I$$

$$M = \mu_0 \pi a^2 n_1 n_2 l \quad \text{mutual inductance}$$

~ o ~


Mutual inductance in practice

(-) elements of electric circuits may interact \Rightarrow unwanted effects

Solution:



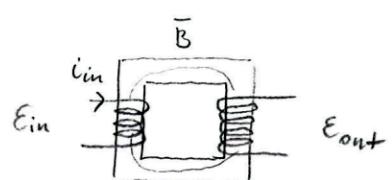
(+) can be used to transform voltage: transformers



$$\text{if } i_{in} \neq 0 \Rightarrow E_{out} = -M \frac{di_{in}}{dt}$$

Self-inductance (inductance)

single loop

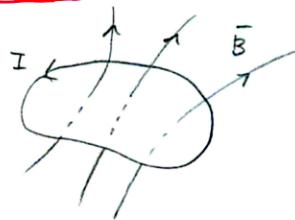


$$\Phi_B \propto I ; \quad \Phi_B = L I$$

↳ self-inductance (or simply "inductance") depending on geometry only


What if $\frac{dI}{dt} \neq 0$? Then $\dot{\Phi}_B \neq 0$ Faraday's law induced emf (direction → Lenz's Rule)

Example

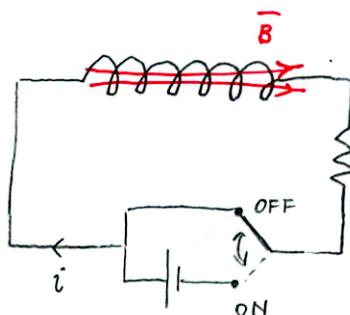


$$\frac{di}{dt} \neq 0 \xrightarrow{B \neq 0} \frac{d\Phi_B}{dt} \neq 0 \xrightarrow[\text{law}]{\text{Faraday's}} E_{\text{induced}}$$


OFF → ON

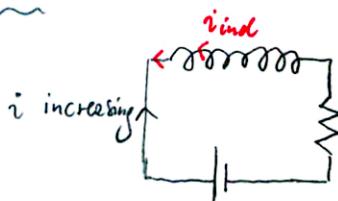

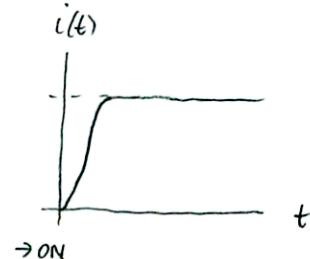
Lenz's rule:
 i_{ind} opposes the change (increase of i)




ON → OFF

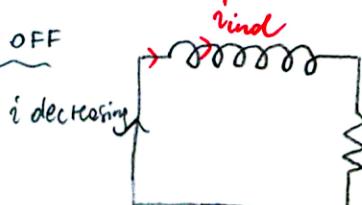

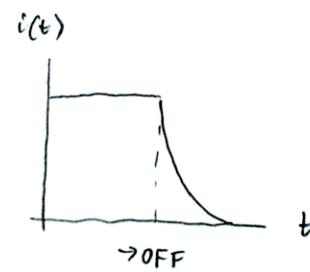Lenz's rule:
 i_{ind} opposes the change (decrease of i)




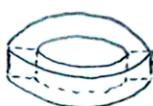Example (inductance of a toroidal coil with rectangular cross-section)




$$\text{Magnetic field inside } B = \frac{\mu_0 I N}{2\pi r} \quad (\text{see rec. class})$$

cross-section

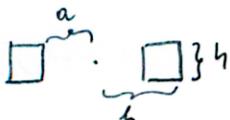

Flux through a single turn
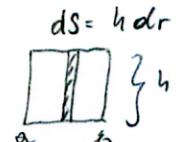
$$\Phi_B^{(1)} = \int \vec{B} \cdot d\vec{S} = \frac{\mu_0 I N}{2\pi r} h \int_a^b \frac{dr}{r} = \frac{\mu_0 I N h}{2\pi} \ln\left(\frac{b}{a}\right)$$




Total flux

$$\Phi_B = N \cdot \Phi_B^{(1)} = \underbrace{\frac{\mu_0 N^2 h}{2\pi} \ln\left(\frac{b}{a}\right)}_L I ;$$

$$L = \frac{\mu_0 N^2 h}{2\pi} \ln\left(\frac{b}{a}\right)$$

Inductive elements in circuits

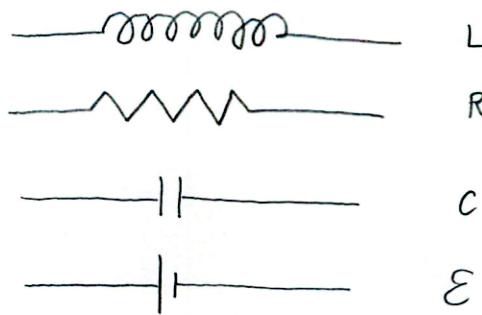

Self inductance and electric circuits

Recall: Electric fields induced by inductive elements are not conservative!

Faraday's law

(assume $R=0$)

$$\oint \bar{E}_{\text{ind}} \cdot d\bar{l} = - L \frac{di}{dt}$$

only \bar{E}_{ind} contributes to circulation ($\bar{E}_{\text{ind}} \neq 0$ only within inductor)

$$\int_a^b \bar{E}_{\text{ind}} \cdot d\bar{l} = - L \frac{di}{dt}$$


$$\int_a^b \bar{E}_{\text{total}} \cdot d\bar{l} = 0 \Rightarrow - \int_a^b \bar{E}_{\text{cons}} \cdot d\bar{l} = - L \frac{di}{dt} \Rightarrow V_{ab} = \int_a^b \bar{E}_{\text{cons}} \cdot d\bar{l} = + L \frac{di}{dt}$$

due to charge accumulated at the ends (a, b)


$V_a - V_b = L \frac{di}{dt}$

→ contribution of an inductive element to Kirchhoff's loop rule
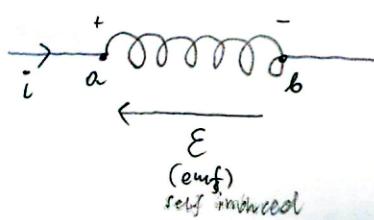
$$\frac{di}{dt} > 0 \Rightarrow V_a > V_b$$



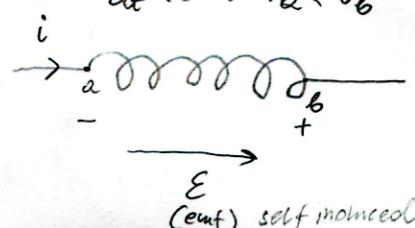
$$\frac{di}{dt} < 0 \Rightarrow V_a < V_b$$




Energy of the magnetic field



$$t=0; i=0$$

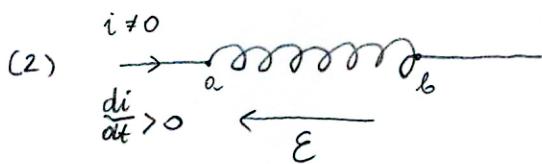

$$t>0; i \neq 0; \frac{di}{dt} > 0$$

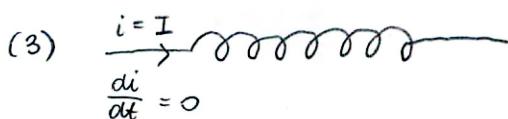

$$t>t_f; i=I = \text{const}; \frac{di}{dt} = 0$$

Analyze (2)

Potential difference across inductive element: $V_{ab} = L \frac{di}{dt}$

Rate at which energy is delivered to inductor: $P = V_{ab} i$
(instantaneous)

$$P = \frac{dU}{dt} = L \frac{di}{dt} i \Rightarrow dU = L i di$$

Total energy delivered from $t=0$ to $t=t_f$ ((1) to (3))

$$U = \int_0^I L i di = \frac{1}{2} L I^2$$

Comments:

(1) If $i = I = \text{const}$ the inductor (with $R=0$) acts as a perfect conductor, but there is energy accumulated during the process of current increase (from 0 to I) that is stored in the inductor


(2) The inductor is "energetically active" only if $\frac{di}{dt} \neq 0$

Compare: Resistor dissipates energy (at rate $i^2 R$) whenever there is current through it ($i \neq 0$)

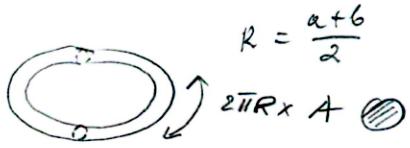Example. Energy stored in a toroidal solenoid. (Assume $b-a \ll a$)

$$L = \frac{\mu_0 N^2 A}{2\pi R}$$

$$U = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi R} I^2$$



Volume of the toroidal coil: $V = 2\pi R A$

Magnetic energy density (energy/unit volume)

$$u = \frac{U}{V} = \frac{1}{2} \mu_0 \frac{N^2 I^2}{(2\pi R)^2}$$

Recall: $B = \frac{\mu_0 I N}{2\pi R}$, so $\frac{N^2 I^2}{(2\pi R)^2} = \frac{B^2}{\mu_0^2}$

Hence

$$u = \frac{B^2}{2\mu_0} \quad (\text{vacuum})$$

→ also valid for other geometries

Comment: Compare with the energy stored in the electric field between plates of a capacitor: $u = \frac{1}{2} \epsilon_0 E^2$

Note. When there is some material (core) in the torus: $\mu = \mu_r \mu_0$

\downarrow
relative magnetic
permeability



CIRCUITS WITH INDUCTIVE ELEMENTS

① \Rightarrow apply Kirchhoff's rules (valid at any instant of time)

(1) junction rule $\sum i = 0$

(2) loop rule $\sum V = 0$


potential difference across inductor

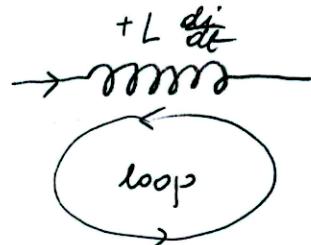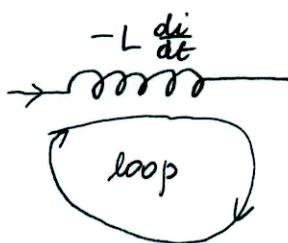

② \Rightarrow step 1 yields a system of (differential) eqns.

③ \Rightarrow solve

RL circuit

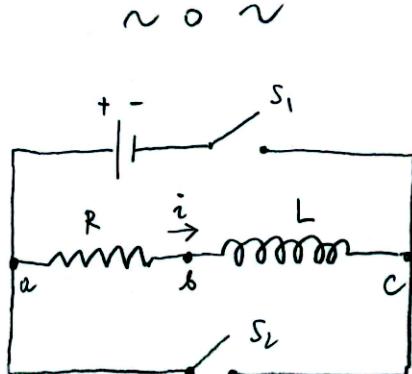

R - the only resistive element

10 S_1, S_2 - open ; closing switch S_1 ,

Initial condition $i(0) = 0$

Let $t > 0$, then $i = i(t)$ - current increasing ($\frac{di}{dt} > 0$)

$$v_{ab} = iR$$

$$v_{bc} = L \frac{di}{dt} > 0$$

$$(v_a > v_b > v_c)$$

Loop rule (Q)

$$-iR - L \frac{di}{dt} + E = 0$$

(1st order ODE, separable)

$$\frac{di}{dt} = \frac{E - iR}{L}$$

$$\text{at } t=0 : \left. \frac{di}{dt} \right|_{t=0} = \frac{E}{L}$$

the larger L , the slower i increases

$$\frac{di}{dt} = -\frac{R}{L} \left(i - \frac{E}{R} \right)$$

$$\int_0^{i(t)} \frac{di}{i - \frac{E}{R}} = -\frac{R}{L} \int_0^t dt$$

$$\ln \left| i - \frac{E}{R} \right| \Big|_0^{i(t)} = -\frac{R}{L} t \quad \Rightarrow \quad \ln \frac{-i(t) + \frac{E}{R}}{\frac{E}{R}} = -\frac{R}{L} t$$

$i(t) = \frac{E}{R} \left(1 - e^{-\frac{R}{L}t} \right)$

Limiting cases:

$$(*) \quad t=0 \Rightarrow i(0)=0, \quad \frac{di}{dt} \Big|_{t=0} = \frac{E}{L}$$

$$(*) \quad t \rightarrow \infty \Rightarrow i(\infty) = \frac{E}{R}, \quad \frac{di}{dt} \Big|_{t \rightarrow \infty} = 0$$

$$t = \frac{L}{R} = \tau \quad \text{time constant for a RL circuit}$$

Energy:	$Ei dt$	- delivered by source	{ }	$Ei dt - i^2 R dt - L idi = 0$
	$-i^2 R dt$	- dissipated in resistor		
	$-L idi$	- stored in inductor		

Exercise: Calculate the total energy delivered, dissipated & stored (see calculations for RC circuit)


2° S_1 closed, S_2 open $\longrightarrow S_1$ open, S_2 closed

initial condition $i(0) = I_0$

Now for $t > 0$, $i = i(t)$

$$V_{ab} = iR$$

$$V_{bc} = L \frac{di}{dt} < 0$$

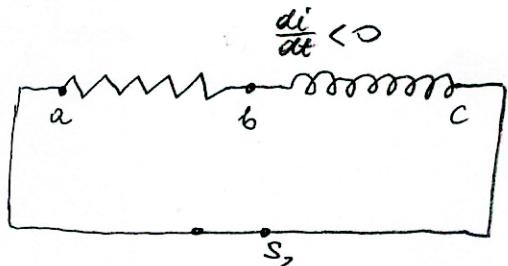


Loop rule \odot

$$-iR - L \left(\frac{di}{dt} \right) < 0 \Rightarrow \frac{di}{dt} + \frac{R}{L} i = 0$$

Solution:

$$i(t) = I_0 e^{-\frac{R}{L}t}$$


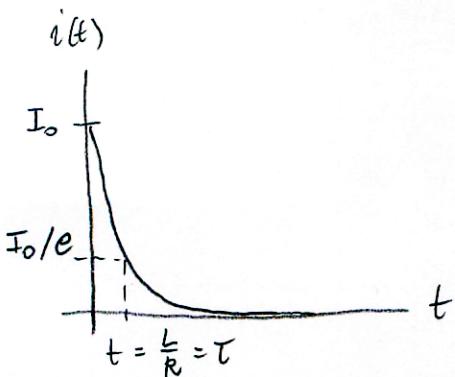


Cf. Discussion of the discharging process in a RC circuit (however, here: energy stored in inductor's magnetic field)

LC circuit

Fig. 1

(30, 14)

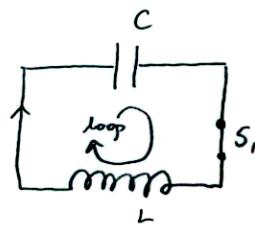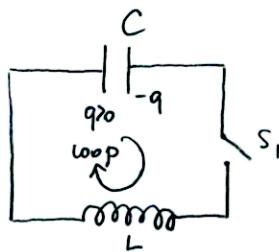

At $t=0$ close switch S_1 : $i(0)=0$ $q(0)=Q_0$ $\left\{ \begin{array}{l} \text{initial conditions} \\ \text{assume positive direction of the current} \end{array} \right.$

Kirchhoff's loop rule (assume positive direction of the current)

$$-\frac{q}{C} - L \frac{di}{dt} = 0$$

$$\text{But } i = \frac{dq}{dt}$$

$$\frac{d^2q}{dt^2} + \frac{1}{LC} q = 0$$

(2nd order linear homogeneous ODE with constant coeffs.)

Solution ($\omega_0 = \sqrt{1/LC}$)

$$q(t) = A \sin \omega_0 t + B \cos \omega_0 t =$$

$$= C \cos(\omega_0 t + \varphi) \quad \rightarrow \text{general solution}$$

\downarrow to be found from initial conditions

Initial conditions:

$$q(0) = C \cos \varphi = Q_0 \quad \Rightarrow C = Q_0$$

$$i(0) = -\omega_0 C \sin \varphi = 0 \quad \Rightarrow \varphi = 0$$

Particular solution (satisfying the initial conditions)

$$q(t) = Q_0 \cos \omega_0 t$$


Compare: $m\ddot{x} + kx = 0$



$$q(t) \leftrightarrow x(t) = C \cos(\omega_0 t + \varphi)$$

$$i(t) \leftrightarrow v(t) = \dot{x}(t)$$

harmonic oscillator

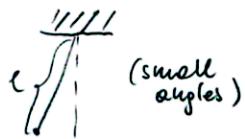


$$\omega_0 = \sqrt{k/m}$$

$$\omega_0 = \sqrt{\frac{k}{m}}$$

Any shape: $\frac{dU}{dx} = 0$ at equilibrium

$$U(x) = U(x_0) + U'(x_0)(x-x_0) + \frac{1}{2} U''(x_0)(x-x_0)^2 \dots$$

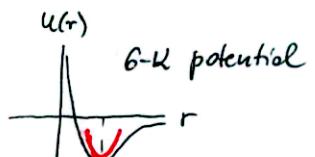
$$\approx U(x_0) + \frac{1}{2} U''(x_0)(x-x_0)^2$$



Results:

$$q(t) = Q_0 \cos \omega_0 t$$
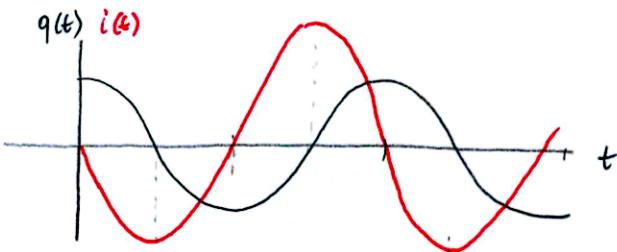
$$i(t) = \dot{q}(t) = -Q_0 \omega_0 \sin \omega_0 t$$




Energy (any instant t)

$$\begin{aligned} \frac{1}{2} L i^2 + \frac{q^2}{2C} &= \frac{L}{2} (Q_0 \omega_0)^2 \sin^2 \omega_0 t + \frac{1}{2C} Q_0^2 \cos^2 \omega_0 t \stackrel{\omega_0 = (LC)^{-\frac{1}{2}}}{=} \\ &= \frac{L}{2} Q_0^2 \frac{1}{LC} \sin^2 \omega_0 t + \frac{1}{2C} Q_0^2 \cos^2 \omega_0 t = \\ &= \frac{Q_0^2}{2L} (\sin^2 \omega_0 t + \cos^2 \omega_0 t) = \frac{Q_0^2}{2L} = \text{const.} \end{aligned}$$

$\sim 0 \sim$

LRC circuit

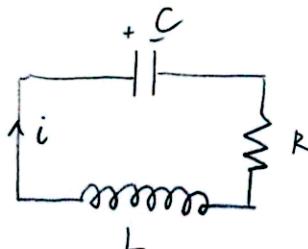

Initial conditions:

$$\begin{aligned} \text{e.g., } q(0) &= Q_0 \\ i(0) &= 0 \end{aligned}$$

loop rule

$$-iR - L \frac{di}{dt} - \frac{q}{C} = 0$$

Again $i = \dot{q}$


$$\ddot{q} + \frac{R}{L} \dot{q} + \frac{1}{LC} q = 0$$

2nd order linear homogeneous
with constant coeffs

Solution

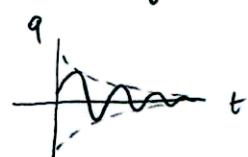
(1) underdamped regime ($R < \sqrt{4L/C}$) [roots of char. eqn. complex]

$$q(t) = A e^{-\frac{R}{2L}t} \cos \left(\sqrt{\omega_0^2 - \frac{R^2}{4L^2}} t + \varphi \right)$$



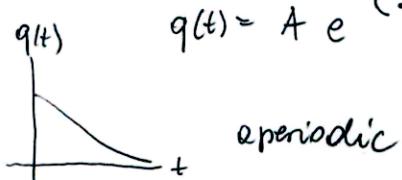(2) overdamped regime ($R > \sqrt{4L/C}$) [roots of char. eqn. real & different]

$$q(t) = A e^{-(\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} - \omega_0^2})t} + B e^{-(\frac{R}{2L} - \sqrt{\frac{R^2}{4L^2} - \omega_0^2})t}$$



(3) critical damping ($R = \sqrt{4L/C}$) $q(t) = A e^{-\frac{R}{2L}t} + B t e^{-\frac{R}{2L}t}$ [roots real & equal]